

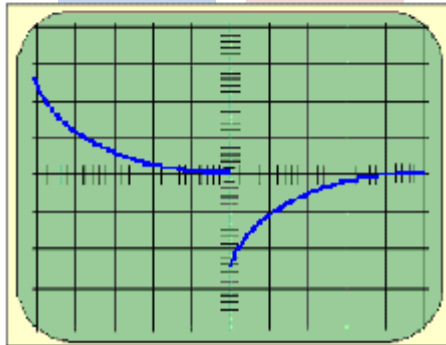
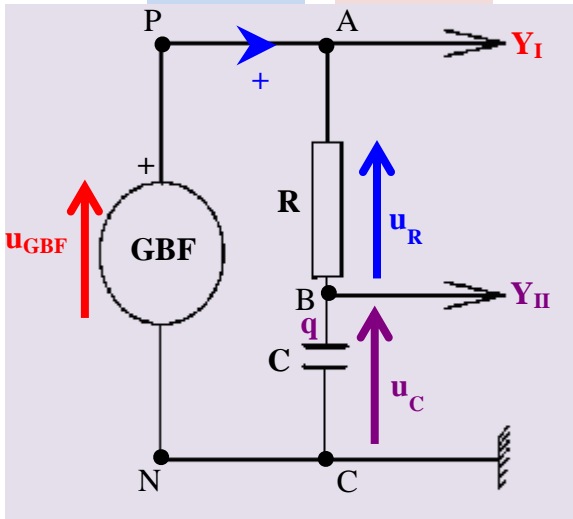


R, C série

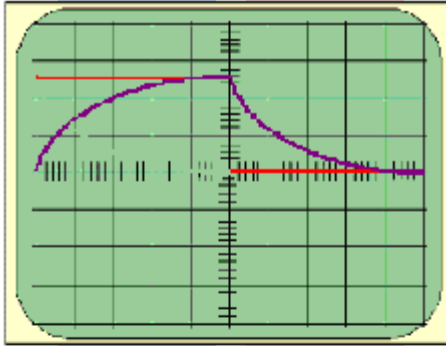

Comparaison R, C et R, L série

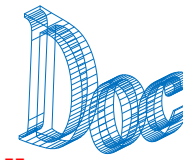

$$u_{AB} + u_{BC} = u_{PN}; \quad u_R + u_{BC} = u_{GBF}; \quad Ri + u_{BC} = u_{GBF}$$

▪ R, C série : $u_{BC} = u_C$

$$u_C = \frac{q}{C}; \quad i = \frac{dq}{dt}$$

$$i = C \frac{du_C}{dt}$$

$$RC \frac{du_C}{dt} + u_C = u_{GBF}$$

$$RC u'_C + u_C = u_{GBF}$$

$$u = u_C \quad \tau = RC$$

▪ R, L série : $u_{BC} = u_L$

$$u_L = L \frac{di}{dt}$$

$$u_L = \frac{L}{R} \frac{du_R}{dt}$$

$$u_R + \frac{L}{R} \frac{du_R}{dt} = u_{GBF}$$

$$u_R + \frac{L}{R} u'_R = u_{GBF}$$

$$u = u_R \quad \tau = \frac{L}{R}$$

$$u_{GBF} = 0$$

$$u_C = E_0 e^{-\frac{t}{RC}}$$

$$u_R = -E_0 e^{-\frac{t}{RC}}$$

$$u'_R = k_1 e^{-\frac{t}{\tau}}$$

$$u_R = E_0 e^{-\frac{R}{L} t}$$

$$u_L = -E_0 e^{-\frac{R}{L} t}$$

$$u_{GBF} = E$$

$$u_C = E \left(1 - e^{-\frac{t}{RC}}\right)$$

$$u_R = E e^{-\frac{t}{RC}}$$

$$u'_R = k_2 e^{-\frac{t}{\tau}}$$

$$u_R = E \left(1 - e^{-\frac{R}{L} t}\right)$$

$$u_L = E e^{-\frac{R}{L} t}$$

R, L série

